

**APPENDIX - A**  
**SMITH CHART**  
**AND ITS APPLICATIONS**

# APPENDIX A


## SMITH CHART AND ITS APPLICATIONS

### Problem A.1

$$\hat{z}_1 = \frac{40 + j30}{50} = 0.8 + j0.6, \quad \hat{z}_2 = \frac{25 - j36}{50} = 0.5 - j0.72$$

$$\hat{z}_3 = \frac{j50}{50} = j1, \quad \hat{z}_4 = \frac{60}{50} = 1.2$$

IMPEDANCE OR ADMITTANCE COORDINATES

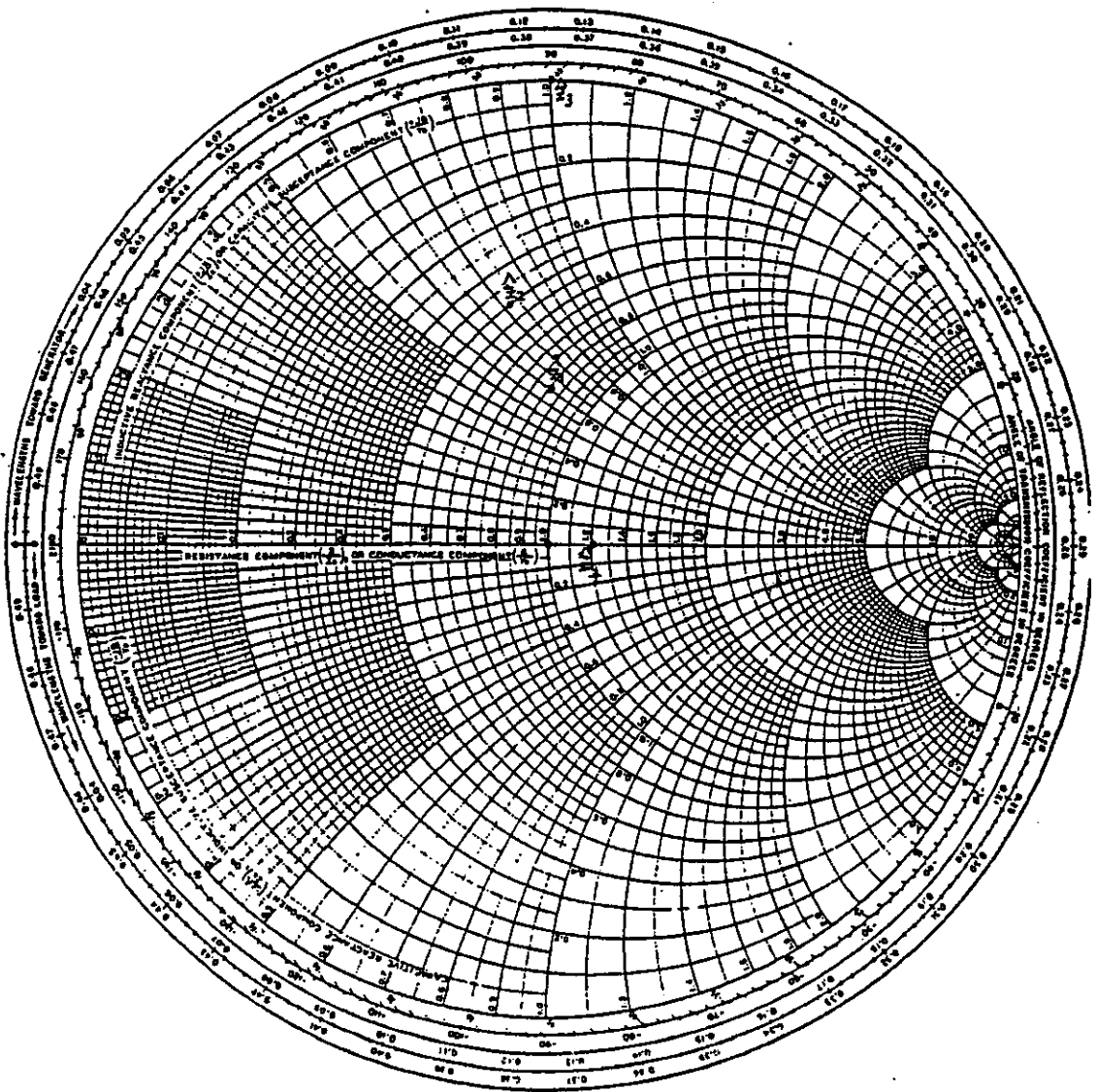


# Problem A.2

$$\hat{Z} = 120 + j280 \Omega, \hat{Z}_c = 100 \Omega$$

$$\hat{z} = \frac{120 + j280}{100} = 1.2 + j2.8$$

From the Smith chart,  $\hat{y} = 0.13 - j0.3$  or  $\hat{Y} = 1.3 \times 10^{-3} - j3 \times 10^{-3}$

IMPEDANCE OR ADMITTANCE COORDINATES

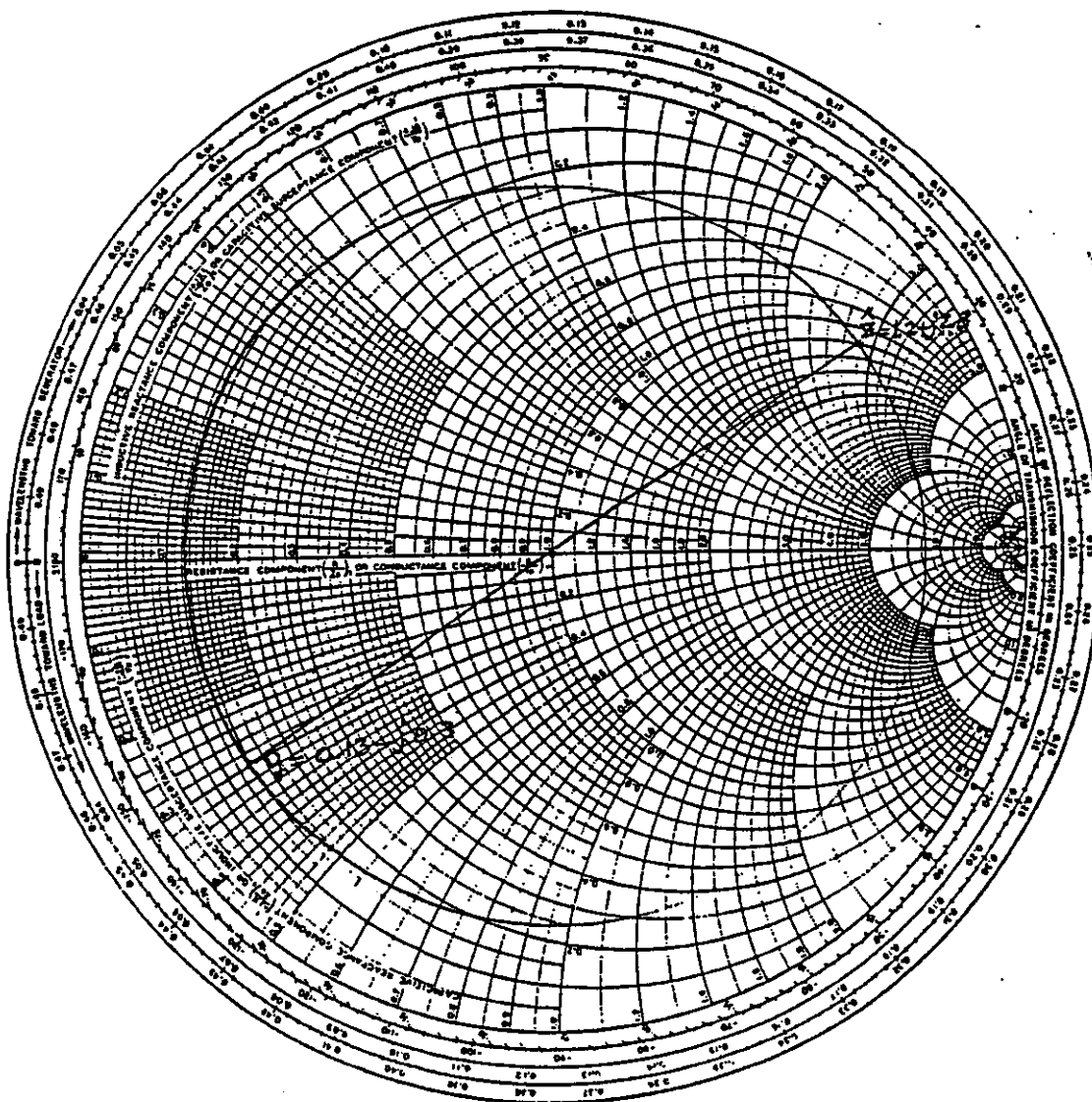

### Problem A.3


$$l = \lambda/4, \quad R_c = 75 \Omega, \quad \hat{Z}_1 = 50 + j25 \Omega, \quad \hat{Z}_2 = 40 - j40 \Omega$$

$$\hat{z}_1 = \frac{50 + j25}{75} = 0.67 + j0.33, \quad \hat{z}_2 = \frac{40 - j40}{75} = 0.53 - j0.53$$

From Smith chart  $\hat{Z}_{L_1} = 1.19 + j0.6$  or  $\hat{Z}_{L_1} = 89.25 - j45 \Omega$

$$\hat{\rho}_{R_1} = 0.278 \angle -56.5^\circ \quad \hat{\rho}_{S_1} = 0.278 \angle 123.5^\circ$$
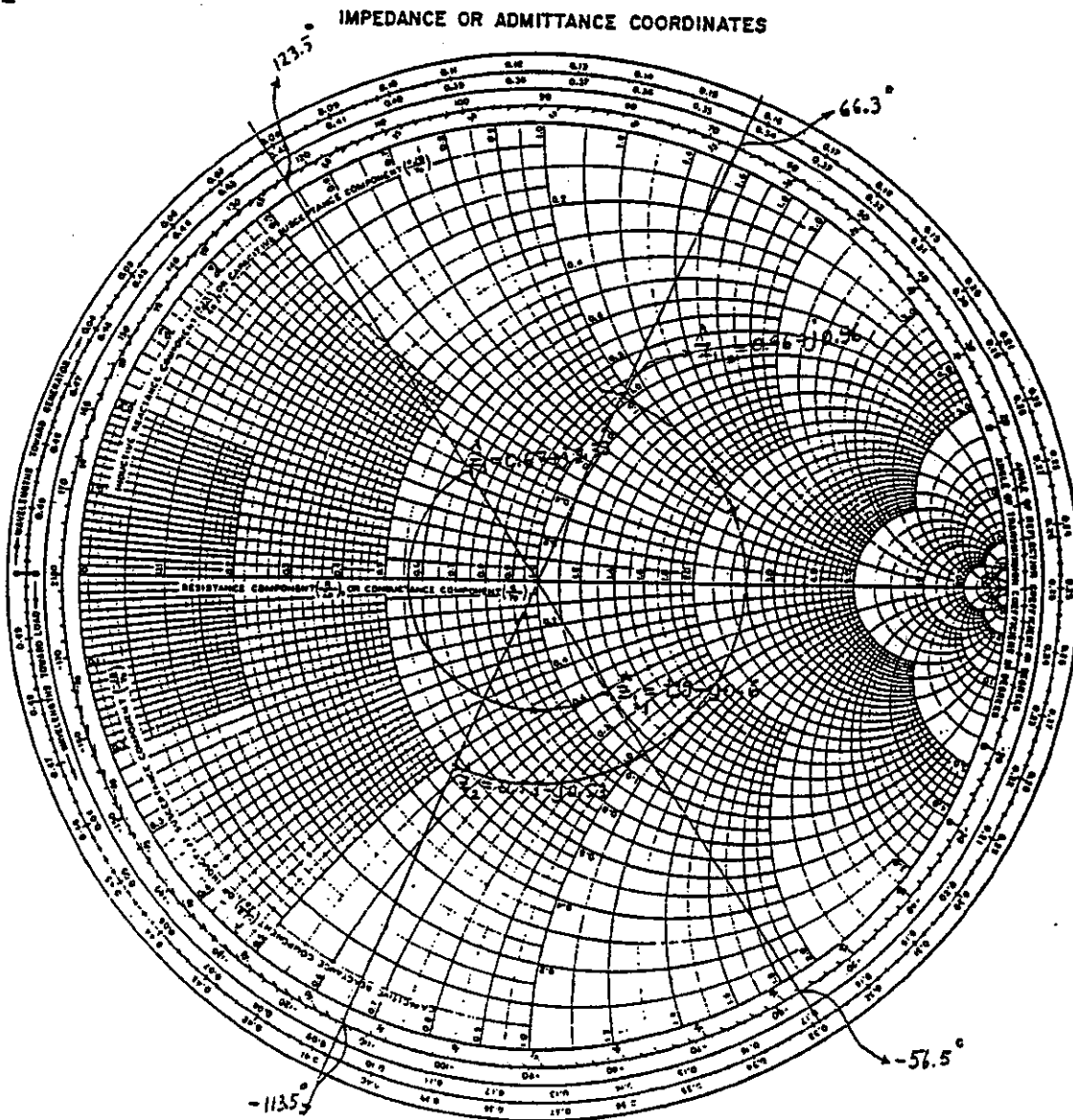
$$\hat{Z}_{L_2} = 0.96 + j0.96 \quad \text{or} \quad \hat{Z}_{L_2} = 72 + j72 \, \Omega, \quad \rho_{R_2} = 0.44 \angle 66.3^\circ, \quad \rho_{S_2} = 0.44 \angle -113.5^\circ$$



# Problem A.4

$$R_c = 50 \Omega, \quad l = 25 \text{ m}, \quad \hat{Z}_{in} = 45 + j60 \Omega, \quad z = 12 \text{ m}, \quad u_p = 2.6 \times 10^8 \text{ m/s}$$

$$f = 5 \text{ MHz}$$

$$\beta = \frac{2\pi \times 5 \times 10^6}{2.6 \times 10^8} = 0.121 \text{ rad/m} \quad \lambda = \frac{2\pi}{0.121} = 52 \text{ m}.$$


$$\frac{l-z}{\lambda} = \frac{25-12}{52} = 0.25 \quad \text{or} \quad l-z = \frac{\lambda}{4}$$

$$\hat{Z}_{in} = \frac{45 + j60}{50} = 0.9 + j1.2$$

From Smith chart  $\hat{Z}_L = 0.4 - j0.53$  or  $\hat{Z}_L = 20 - j26.5 \Omega$

$$\hat{\rho}_R = 0.544 \angle -117^\circ$$

IMPEDANCE OR ADMITTANCE COORDINATES

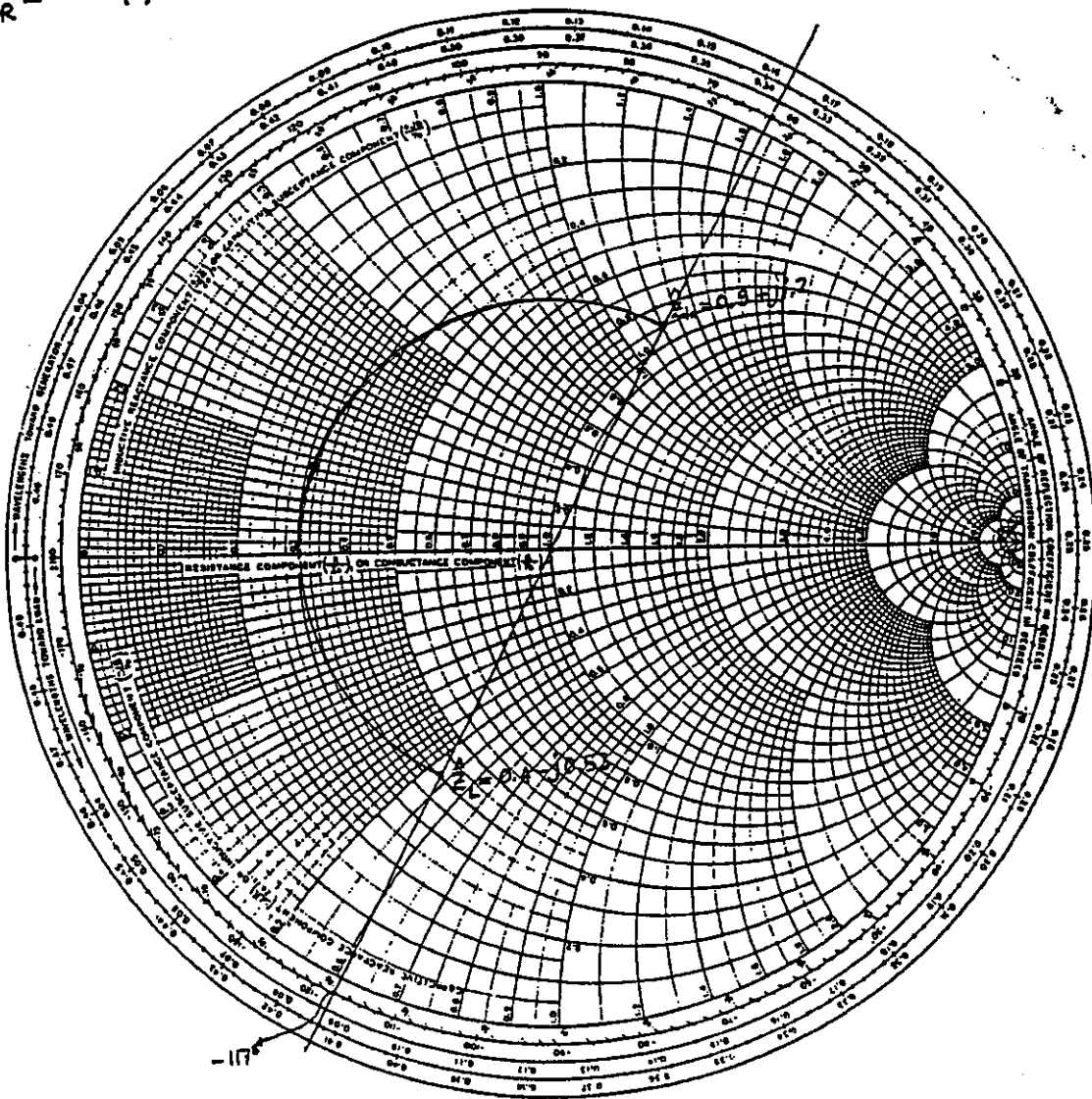

### Problem A.5

$$l = 30\text{m}, R_c = 90\Omega, \mu_p = 2.8 \times 10^8 \text{ m/s}, f = 10 \text{ MHz}$$


$$\hat{Z}_L = 60 \angle 15^\circ \Omega, \hat{z}_L = \frac{60 \angle 15^\circ}{90} = 0.67 \angle 15^\circ = 0.644 + j0.173$$

$$\beta = \frac{2\pi \times 10^7}{2.8 \times 10^8} = 0.224 \text{ rad/m} \quad \lambda = \frac{2\pi}{0.224} = 28 \text{ m}$$

$$\frac{l}{\lambda} = \frac{30}{28} = 1.07 \Rightarrow l = 1.07\lambda$$

From Smith chart  $\hat{Z}_{in} = 0.83 + j0.44$  or  $\hat{Z}_{in} = 74.7 + j39.6 \Omega$
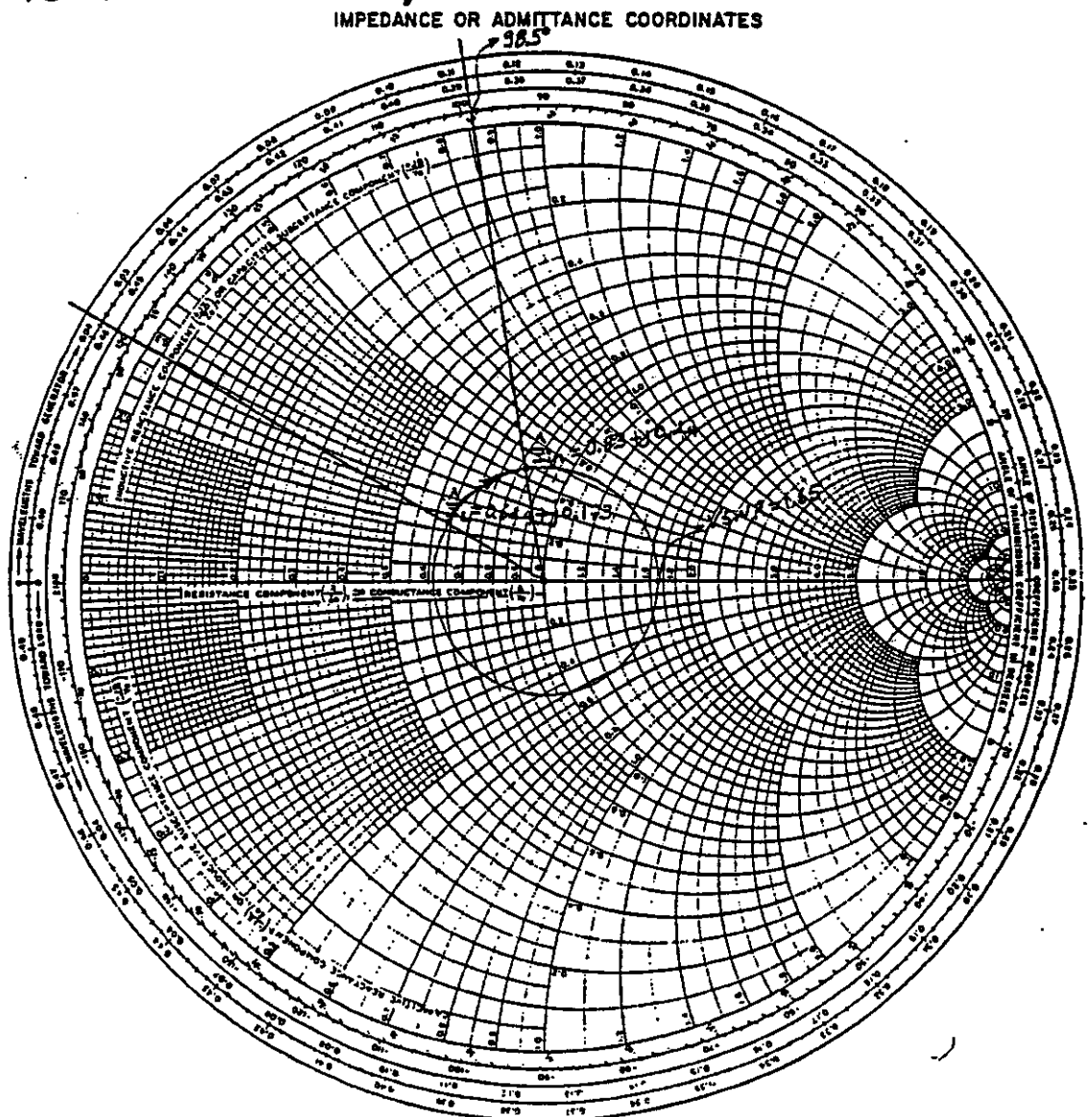
$$\text{VSWR} = 1.65 \text{ and } \hat{\rho}_s = 0.25 \angle 98.5^\circ$$



# Problem A.6

$$l = 2\text{m}, \hat{Z}_c = 75\Omega, u_p = 2.6 \times 10^8 \text{ m/s}, \hat{Z}_L = 120 + j90\Omega$$

$$V_R(t) = 150 \cos(1.26 \times 10^8 t) \text{ V}$$


$$\beta = \frac{1.26 \times 10^8}{2.6 \times 10^8} = 0.485 \text{ rad/m}, \quad \lambda = \frac{2\pi}{0.4}$$

$$\hat{Z}_L = \frac{120 + j90}{75} = 1.6 + j1.2$$

From Smith chart, a)  $\hat{\rho}_R = 0.47 \angle 38.5^\circ, \hat{\rho}(z) = 0.47 e^{j38.5^\circ - j0.97(2-z)}$

b)  $VSWR = 2.8$

IMPEDANCE OR ADMITTANCE COORDINATES

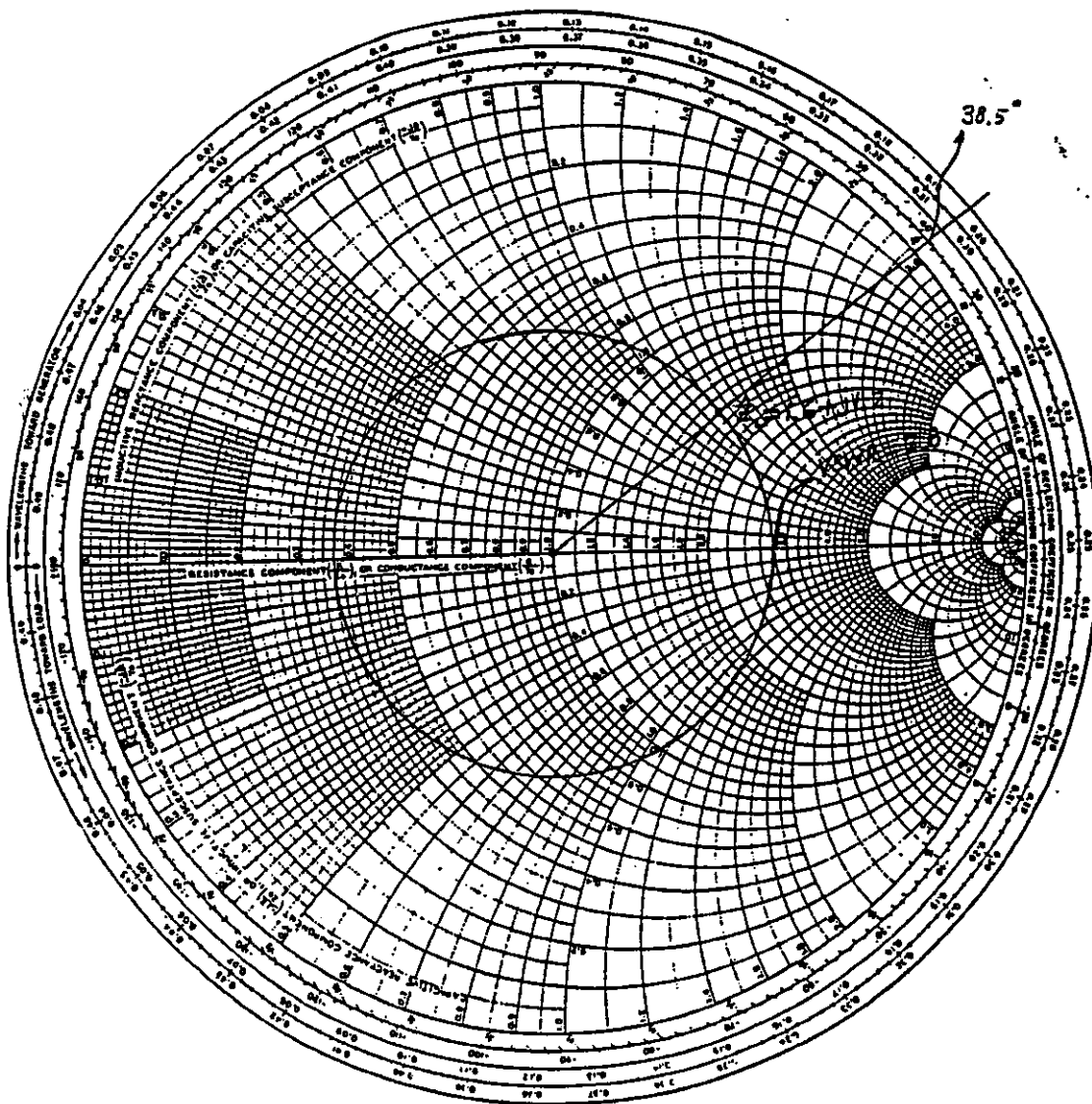

# Problem A.7

$$l = 50 \text{ m} \quad L_x = 0.5 \mu\text{H/m}, \quad C_x = 50 \text{ pF/m}, \quad v_s(t) = 280 \cos(6.28 \times 10^7 t) \text{ V}$$


$$\hat{Z}_L = 250 \Omega \quad \hat{Z}_c = \sqrt{\frac{0.5 \times 10^{-6}}{50 \times 10^{-12}}} = 100 \Omega,$$

$$\beta = 6.28 \times 10^7 \sqrt{0.5 \times 10^{-6} \times 50 \times 10^{-12}} = 0.314 \text{ rad/m} \quad \lambda = \frac{2\pi}{0.314} = 20 \text{ m}$$

$$l = \frac{50}{20} \lambda \quad l = 2.5 \lambda \quad \hat{Z}_L = \frac{250}{100} = 2.5$$

From Smith chart a)  $\hat{P}_R = 0.43 \text{ W}$ , b)  $\hat{Z}_{in} = 250 \Omega$
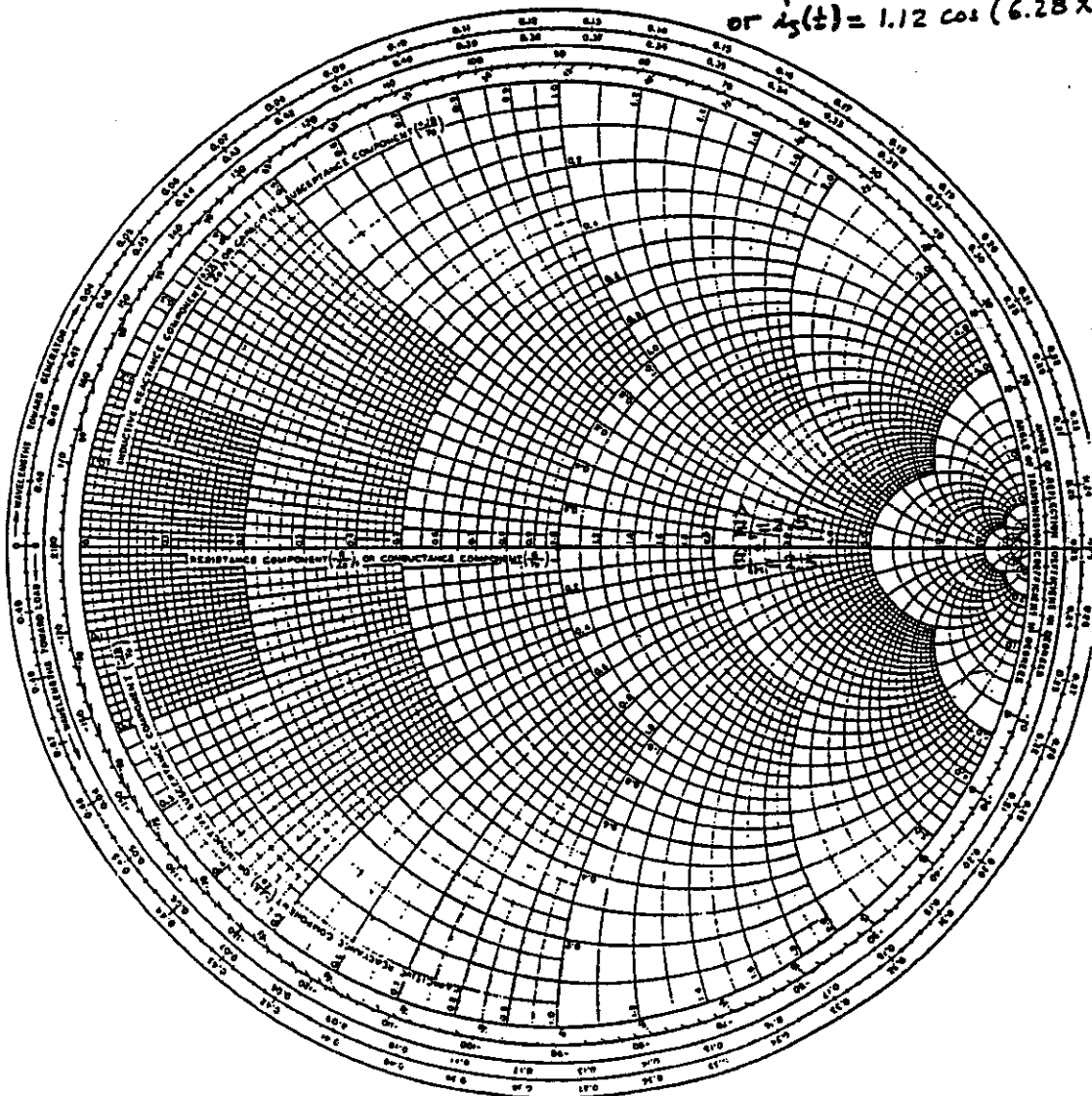
$$\text{IMPEDANCE OR ADMITTANCE COORDINATES } i_s(t) = \frac{280}{250} \cos(6.28 \times 10^7 t) \\ \text{or } i_s(t) = 1.12 \cos(6.28 \times 10^7 t) \text{ A}$$





### Problem A.8


$$\hat{Z}_C = 75 \Omega, \quad v_s(t) = 50 \cos(10^7 t) \text{ V}, \quad i_s(t) = 0.5 \cos(10^7 t - 36.8^\circ) \text{ A}$$

$$\hat{Z}_L = 36.5 + j21.25 \Omega \quad \mu_p = 2.5 \times 10^8 \text{ m/s}$$

$$\hat{Z}_{in} = \frac{50 \angle 0^\circ}{0.5 \angle -36.8^\circ} = 100 \angle 36.8^\circ \Omega = 80 + j60 \Omega \quad \hat{Z}_{in} = \frac{80 + j60}{75} = 1.07 + j0.8$$

$$\hat{Z}_L = \frac{36.5 + j21.25}{75} = 0.487 + j0.283 \quad \beta = \frac{10^7}{2.5 \times 10^8} = 0.04 \text{ rad/m} \quad \lambda = \frac{2\pi}{0.04} = 157 \text{ m}$$

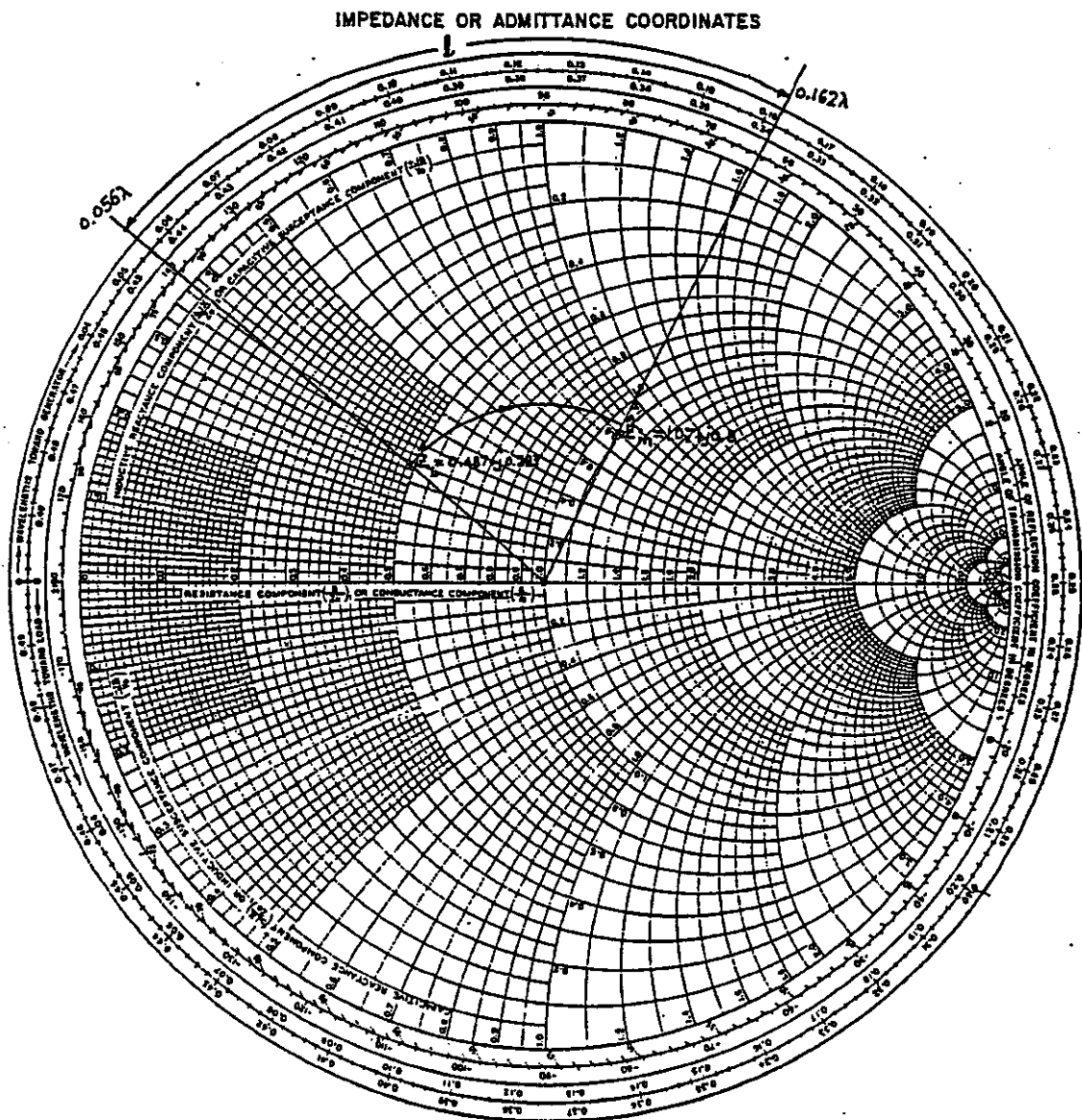From Smith Chart  $l = (0.162 - 0.056)\lambda = 0.106\lambda$ ,  $l = 0.106\lambda = 0.106 \times 157 = 16.64 \text{ m}$



### Problem A.9

$$\hat{Z}_L = 73 + j42.5 \Omega, l = 50 \text{ m}, \hat{Z}_c = 50 \Omega, \tilde{V}_s = 100 \angle 0^\circ (\text{rms}), t_t = 0.2 \mu\text{s}$$

$$f = 950 \text{ kHz}$$


$$u_p = \frac{50}{0.2 \times 10^{-6}} = 2.5 \times 10^8 \text{ m/s}, \quad \beta = \frac{2\pi \times 950 \times 10^3}{2.5 \times 10^8} = 0.024 \text{ rad/m},$$

$$\lambda = \frac{2\pi}{0.024} = 261.8 \text{ m}, \quad l = \frac{50}{261.8} \lambda \Rightarrow l = 0.19 \lambda, \quad \hat{Z}_L = \frac{73 + j42.5}{50} = 1.46 + j0.85$$

$$\text{From Smith chart, } \hat{z}_{in} = 0.73 - j0.62 \text{ or } \hat{Z}_{in} = 36.5 - j31 \Omega = 47.89 \angle -40.34^\circ$$

$$\tilde{I}_s = (100 \angle 0^\circ) / (47.89 \angle -40.34^\circ) = 2.088 \angle 40.34^\circ \text{ A (rms)}$$

IMPEDANCE OR ADMITTANCE COORDINATES

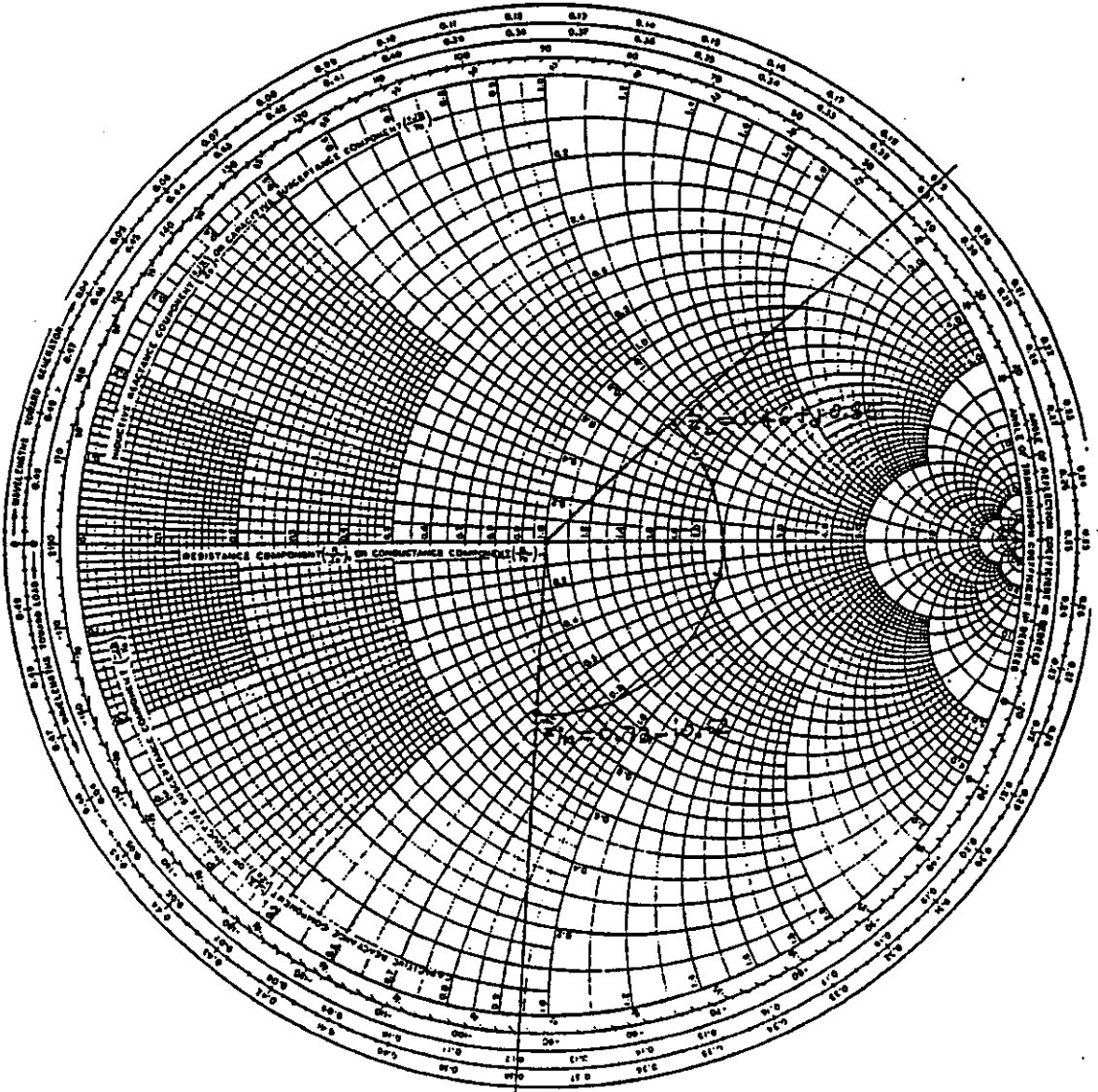

# Problem A.10


$$\hat{Z}_C = 50 \Omega, R_G = 25 \Omega, \hat{Z}_L = 35 - j20 \Omega$$

$$\hat{Z}_L = \frac{35 - j20}{50} = 0.7 - j0.4, \hat{Z}_{in} = R_G = 25 \Omega \text{ for the maximum power transfer.}$$

$$\hat{Z}_{in} = \frac{25}{50} = 0.5$$

$$\text{From Smith Chart } l = (0.5 - 0.408) \lambda = 0.092 \lambda$$

IMPEDANCE OR ADMITTANCE COORDINATES

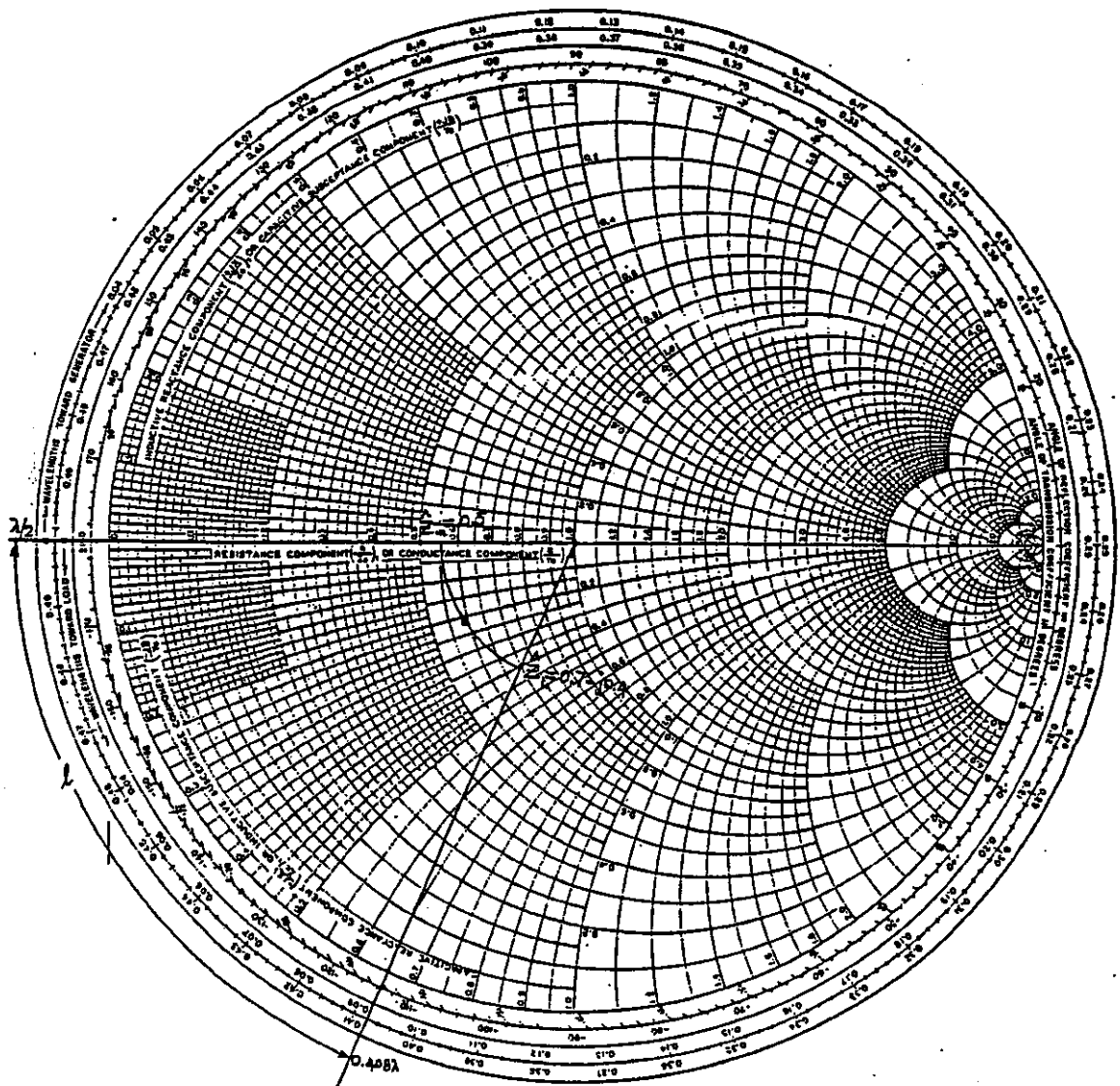


# Problem A.11

From Smith chart  $d = (0.5 - 0.304)\lambda + 0.158\lambda = 0.354\lambda$

$$d = 0.354 \times 157 = 55.58 \text{ m}$$
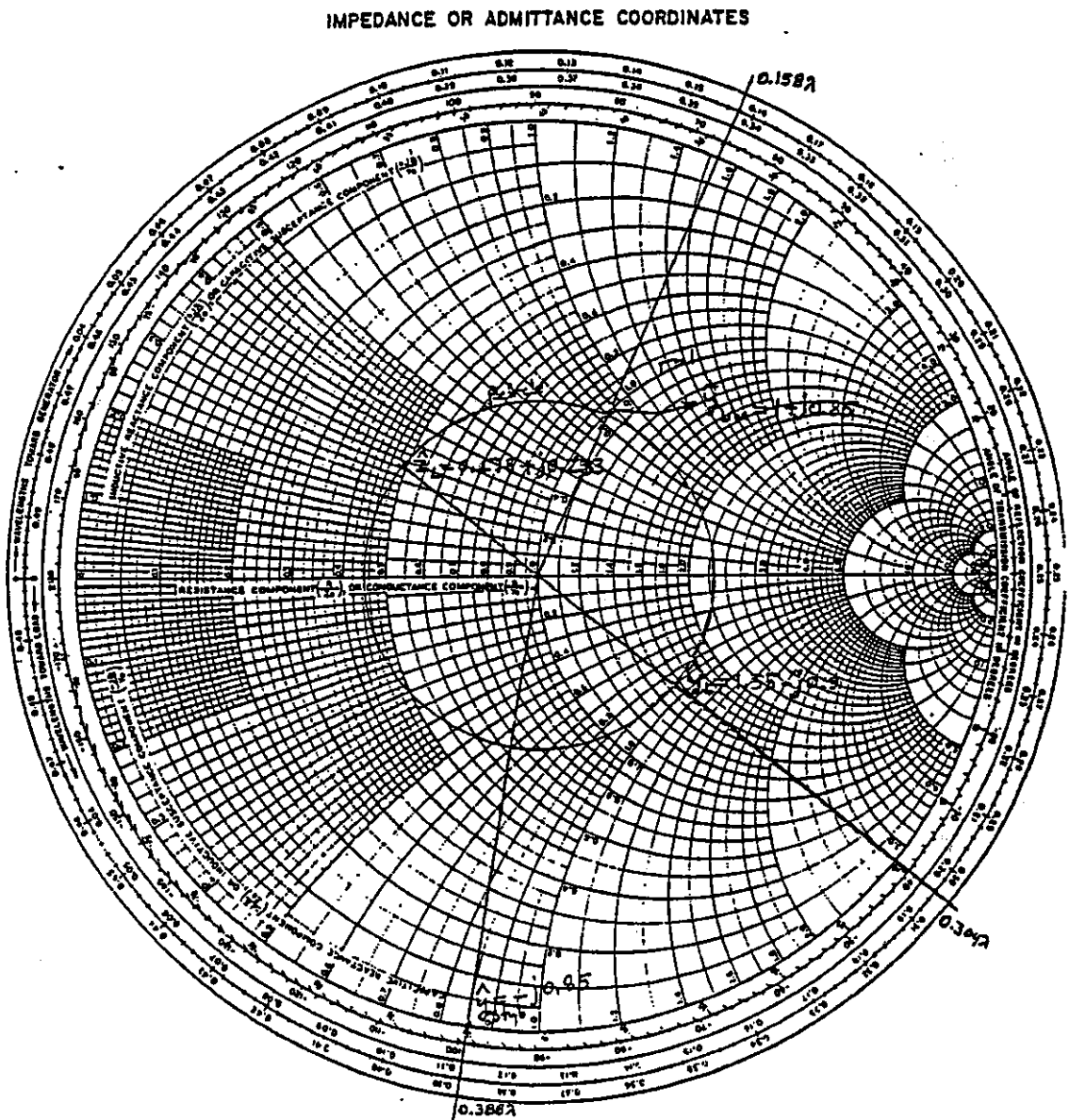
$$l_s = (0.388 - 0.25)\lambda = 0.138\lambda \quad l_s = 0.138 \times 157 = 21.67 \text{ m}$$




# Problem A.12

It is not perfectly matched.

From Smith chart  $d = (0.5 - 0.445)\lambda + 0.156\lambda = 0.211\lambda$

$l_s = (0.392 - 0.25)\lambda \quad l_s = 0.142\lambda$

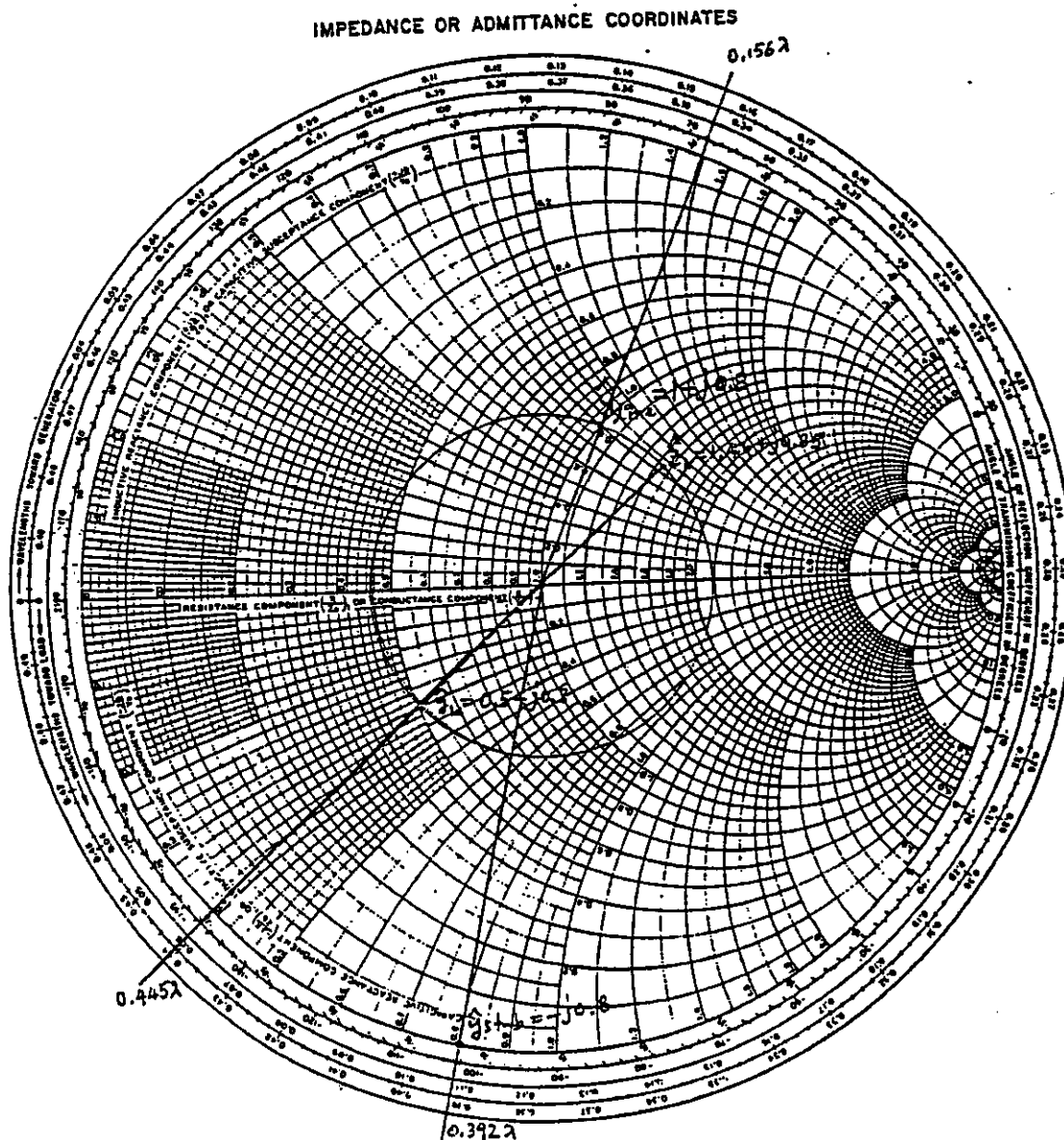$d = 0.211 \times 261.8 = 55.24 \text{ m} \quad , \quad l_s = 0.142 \times 261.8 = 37.18 \text{ m}$



### Problem A.13

$$\hat{Z}_C = 100 \Omega, \quad l = 15 \text{ m} \quad u_p = 2.8 \times 10^8 \text{ m/s} \quad \hat{Z}_L = 250 \Omega, \quad v_g = 35 \cos(8 \times 10^7 t) \text{ V}$$

$$\hat{Z}_G = 20 - j10 \Omega$$

$$\beta = \frac{8 \times 10^7}{2.8 \times 10^8} = 0.286 \text{ rad/m}, \quad \lambda = \frac{2\pi}{0.286} = 21.99 \text{ m}, \quad l = \frac{15\lambda}{21.99} = 0.682\lambda$$

$$\hat{Z}_L = \frac{250}{100} = 2.5$$

a) From Smith chart  $\hat{Z}_S = 0.46 - j0.37$  or  $\hat{Z}_S = 46 - j37 \Omega$

$$\tilde{I}_S = \frac{35}{20 - j10 + 46 - j37} \cong 0.353 + j0.247 = 0.43 \angle 34.98^\circ \text{ A}$$

$$\tilde{V}_S = \hat{Z}_S \tilde{I}_S = 25.51 \angle -3.17^\circ \text{ V}$$

$$\hat{S}_S = \frac{1}{2} (25.51 \angle -3.17^\circ) (0.43 \angle -34.98^\circ)^* = 4.313 - j3.388 \text{ VA}$$

b)  $\tilde{V}_R = \tilde{V}_S \cos(\beta l) - j \hat{Z}_L \tilde{I}_S \sin(\beta l) = 46.484 \angle 135.17^\circ \text{ V}$

$$\tilde{I}_R = \frac{\tilde{V}_R}{\hat{Z}_L} = 0.186 \angle 135.17^\circ \text{ A}$$

$$\hat{S}_R = \frac{1}{2} \tilde{V}_R \tilde{I}_R^* = 4.323 \text{ VA} \quad P_R = 4.323 \text{ W}$$

c)  $z = 5 \text{ m}$  from the supply  $\hat{z} = \frac{5}{21.99} \lambda = 0.2273\lambda$

From Smith chart  $\hat{Z}(5\text{m}) = 1.8 + j1$  or  $\hat{Z}(5\text{m}) = 180 + j100 \Omega$

$$\tilde{V}(5\text{m}) = \tilde{V}_S \cos[\beta(l-5)] - j \hat{Z}_L \tilde{I}_S \sin[\beta(l-5)] = 19.531 \angle -154.35^\circ \text{ V}$$

$$\tilde{I}(5\text{m}) = -j \frac{1}{\hat{Z}_L} \tilde{V}_S \sin[\beta(l-5)] + \tilde{I}_S \cos[\beta(l-5)] = 0.461 \angle -138.079^\circ \text{ A}$$

$$\hat{S}(5\text{m}) = \frac{1}{2} \tilde{V}(5\text{m}) \tilde{I}(5\text{m})^* = 4.32 - j1.261 \text{ VA}$$

d)  $z = 10\text{ m}$  from the supply  $z = \frac{10}{21.99} \lambda = 0.455 \lambda$


From Smith chart  $\hat{z}(10\text{m}) = 0.405 - j0.12$  or  $\hat{z}(10\text{m}) = 40.5 - j12 \Omega$

$$\tilde{V}(10\text{m}) = \tilde{V}_s \cos[\beta(l-10)] - j\hat{z}_c \tilde{I}_s \sin[\beta(l-10)] = 44.951 \angle -51.435^\circ \text{ V}$$

$$\tilde{I}(10\text{m}) = -j \frac{1}{\hat{z}_c} V_s \sin[\beta(l-10)] + \tilde{I}_s \cos[\beta(l-10)] = 0.22 \angle -80.71^\circ \text{ A}$$

$$\hat{S}(10\text{m}) = \frac{1}{2} \tilde{V}(10\text{m}) \tilde{I}^*(10\text{m}) = 4.32 + j2.42 \text{ VA}$$

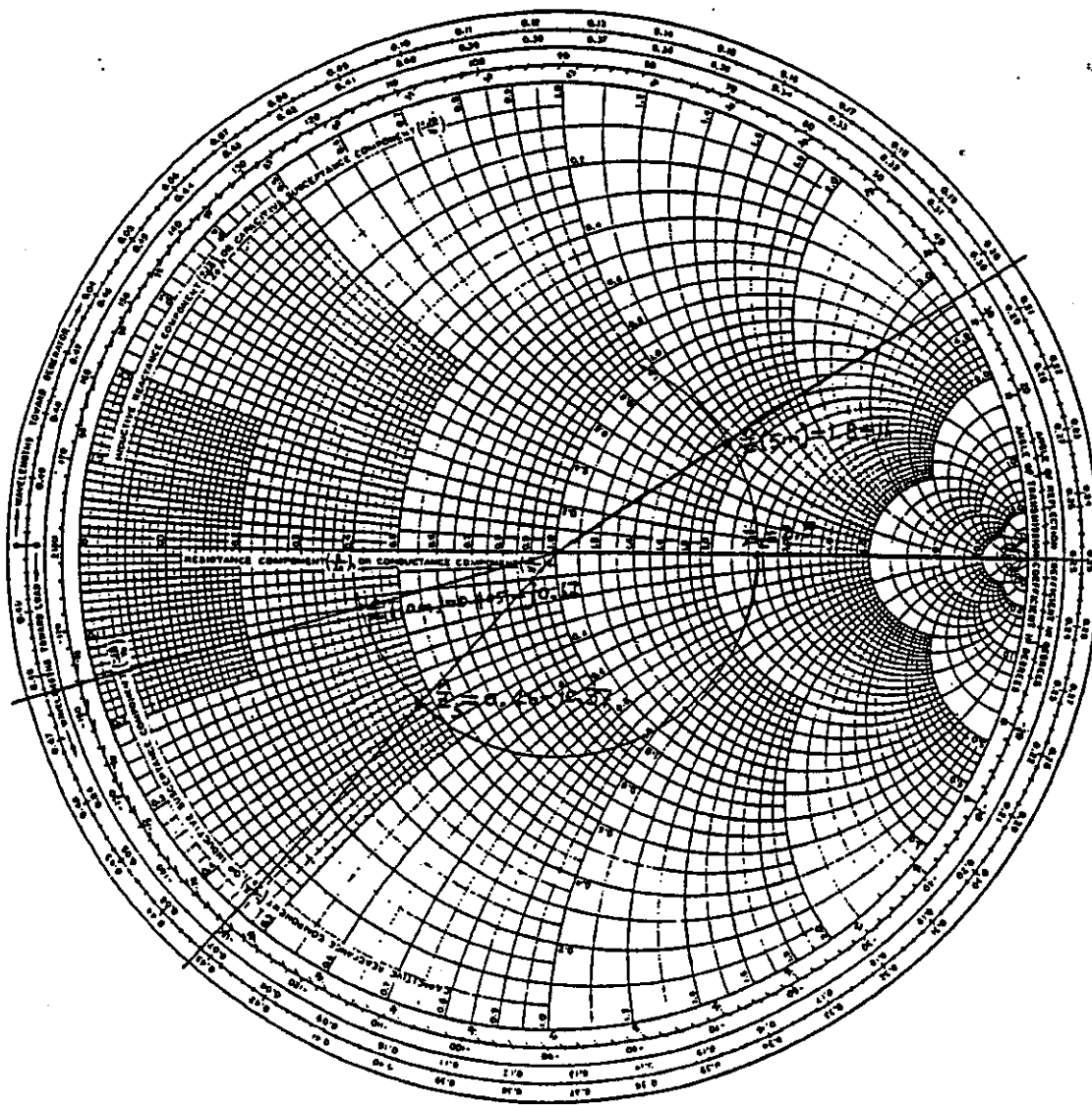e)  $\Delta V = V_s - V_R = 25.51 - 46.484 = -20.974$   
 IMPEDANCE OR ADMITTANCE COORDINATES



# Problem A.14

$$\hat{Z}_C = 50 \Omega, \quad l = 100 \text{ m}, \quad \hat{Z}_L = 40 - j100 \Omega, \quad t_L = 0.5 \mu\text{s}, \quad f = 20 \text{ MHz}$$


$$\beta = \frac{2\pi \times 20 \times 10^6}{(100 / 0.5 \times 10^{-6})} = 0.628 \text{ rad/m}, \quad \lambda = \frac{2\pi}{0.628} = 10 \text{ m}, \quad l = \frac{100}{10} \lambda = 10\lambda$$

$$\hat{z}_L = \frac{40 - j100}{50} = 0.8 - j2$$

$$\text{From Smith chart } d = (0.192 - 0.066) \lambda = 0.126 \lambda, \quad d = 0.126 \times 10 = 1.26 \text{ m}$$

$$l_s = (0.321 - 0.25) \lambda = 0.071 \lambda, \quad l_s = 0.071 \times 10 = 0.71 \text{ m}$$

IMPEDANCE OR ADMITTANCE COORDINATES

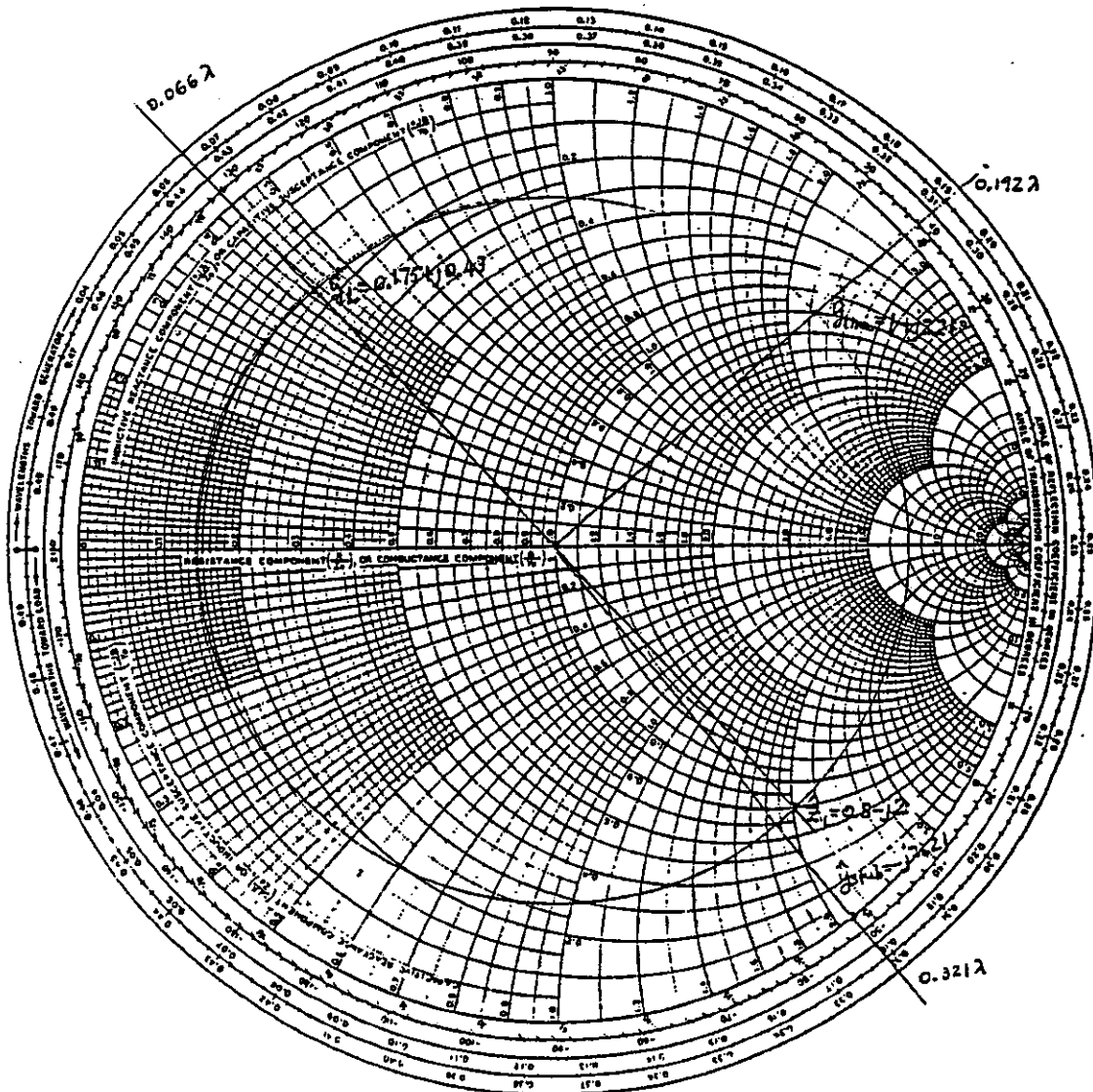



# Problem A.15

$$l = 15\text{m}, f = 125\text{MHz}, \hat{Z}_L = 150 + j225\Omega, d_c = 2.5\text{mm}, d_o = 6\text{mm}$$

$$L_\lambda = \frac{4\pi \times 10^{-7}}{2\pi} \ln \frac{3}{1.25} = 1.75 \times 10^{-7} \text{H/m}, C_\lambda = \frac{2\pi \times 8.85 \times 10^{-12}}{\ln \frac{3}{1.25}} = 6.35 \times 10^{-11} \text{F/m}$$

$$Z_c = \sqrt{\frac{1.75 \times 10^{-7}}{6.35 \times 10^{-11}}} = 52.5\Omega \quad u_p = \frac{1}{\sqrt{1.75 \times 10^{-7} \times 6.35 \times 10^{-11}}} = 3 \times 10^8 \text{m/s}$$

$$\beta = \frac{2\pi \times 125 \times 10^6}{3 \times 10^8} = 2.62 \text{rad/m} \quad \lambda = \frac{2\pi}{2.62} = 2.4\text{m} \quad l = \frac{15}{2.4} \lambda = 6.25\lambda$$

$$\hat{Z}_L = \frac{150 + j225}{52.5} = 2.86 + j4.29$$

$$\text{From Smith chart} \quad d = (0.5 - 0.474)\lambda + 0.2\lambda = 0.226\lambda$$

$$d = 0.226 \times 2.4 = 0.5424\text{m}$$

$$l_s = (0.305 - 0.25)\lambda = 0.055\lambda \quad l_s = 0.055 \times 2.4 = 0.132\text{m}$$

IMPEDANCE OR ADMITTANCE COORDINATES

