
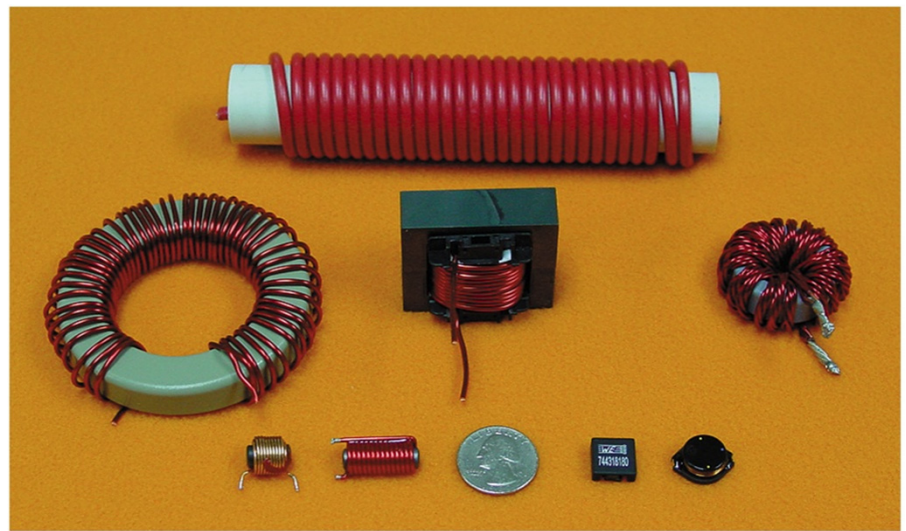


# Capacitors and Inductors
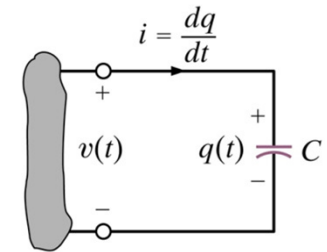
## *Individual Characteristics and Combinations*



# Key Points



## 1. A **capacitor** as a circuit element is characterized by:

- ❑ The instantaneous current through the capacitor depends on the rate of change of the voltage across the capacitor:  $i_C(t) = C \frac{dv_C(t)}{dt}$
- ❑ The instantaneous power is:  $p_C(t) = v_C(t)i_C(t)$
- ❑ The instantaneous stored energy is:  $w_C(t) = \int_{-\infty}^t p_L(t')dt' = \frac{1}{2}Cv_C^2(t)$
- ❑ The voltage across a capacitor cannot change instantaneously, i.e.,  $i_C = C \frac{dv_C}{dt} \neq \infty$
- ❑ After the initial charging up, a capacitor will look like an open-circuit ( $i_C = 0$ ) to a DC (direct current) source
- ❑ Series capacitors have the same charges on their plates, thus the equivalent is:


$$C_{eqSeries} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)^{-1}$$

- ❑ Parallel capacitors have the same voltage across them, thus the equivalent is:

$$C_{eqParallel} = C_1 + C_2 + \dots + C_n$$
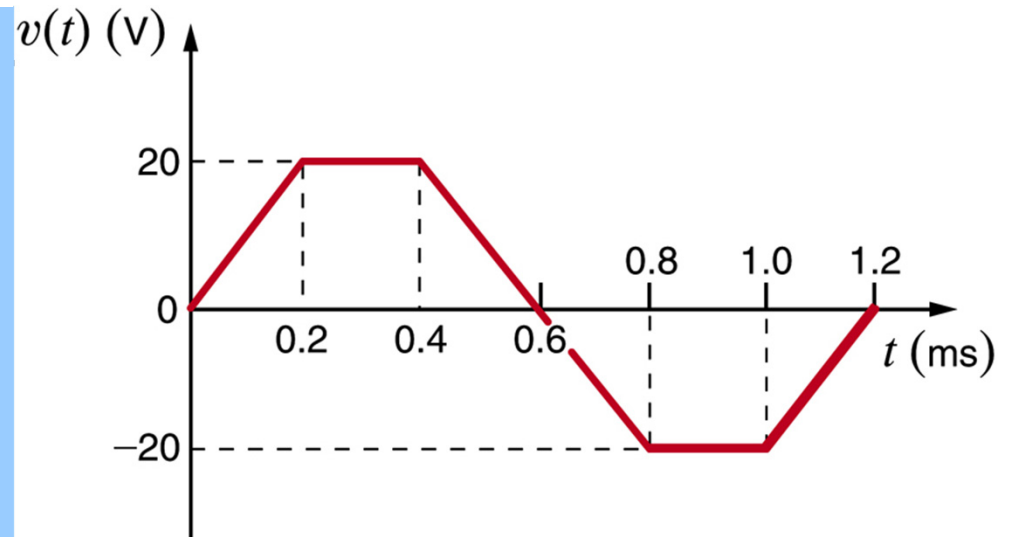
## Clicker

The voltage across a  $1 \mu\text{F}$  capacitor is shown to the right. What is the current through the capacitor at  $t = 0.9 \text{ ms}$ ?





- A.**  $i_C = 0 \text{ A}$                       **D.**  $i_C = -0.022 \text{ A}$
- B.**  $i_C = 0.022 \text{ A}$                       **E.**  $i_C = 2.2 \text{ mA}$
- C.**  $i_C = -20 \text{ A}$


# Example 1:
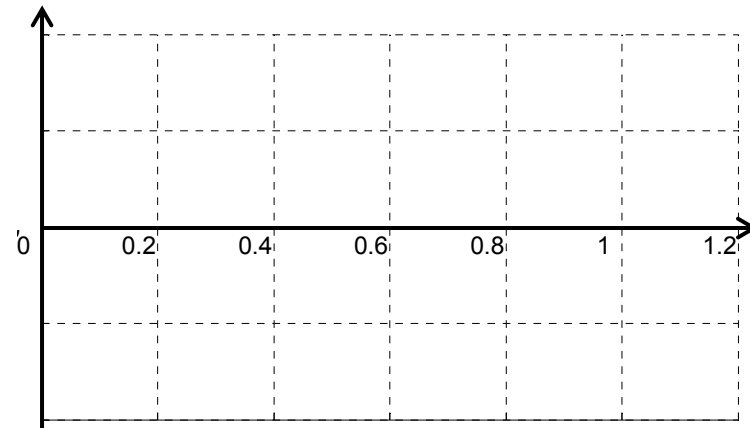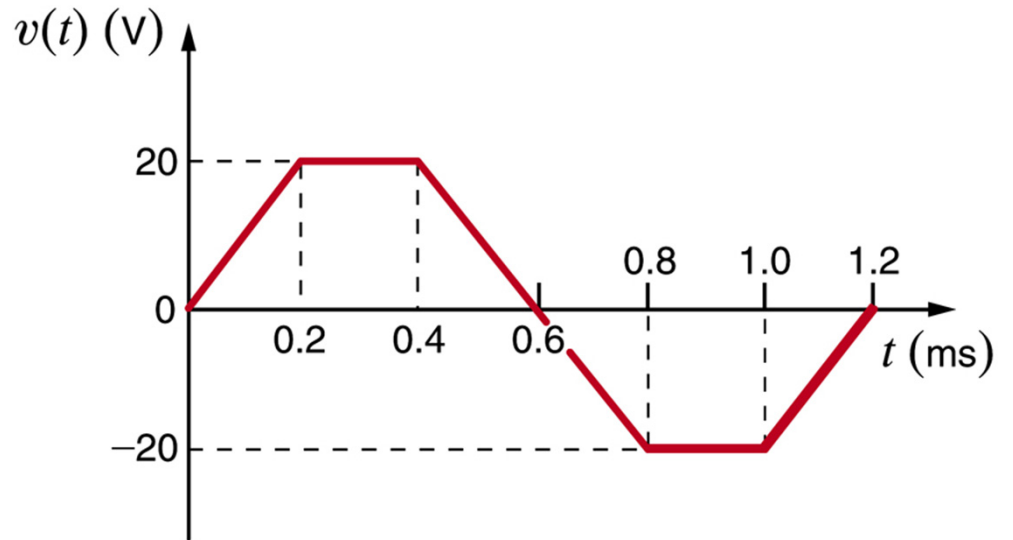
## Current, Power, and Energy in a Capacitor

The voltage across a  $1 \mu\text{F}$  capacitor is shown to the right. Draw the current waveform,  $i(t)$



## Key Points (cont'd)

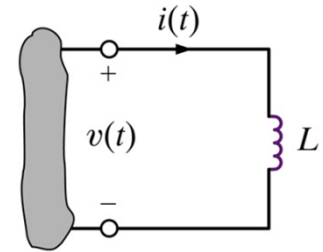

### 2. An **inductor** as a circuit element is characterized by:

- ❑ The instantaneous voltage across the inductor depends on the rate of change of the current through the inductor:  $v_L(t) = L \frac{di_L(t)}{dt}$
- ❑ The instantaneous power is:  $p_L(t) = v_L(t)i_L(t)$
- ❑ The instantaneous stored energy is:  $w_L(t) = \int_{-\infty}^t p_L(t')dt' = \frac{1}{2} Li_L^2(t)$
- ❑ The current through an inductor cannot change instantaneously, i.e.,  $v_L = L \frac{di_L}{dt} \neq \infty$
- ❑ After the initial “charging up”, an inductor will look like a short-circuit ( $v_L = 0$ ) to a DC (direct current) source
- ❑ Series inductors have the same current through them, thus the equivalent is:


$$L_{eqSeries} = L_1 + L_2 + \dots + L_n$$

- ❑ Parallel inductors have the same voltage across them, thus the equivalent is:

$$L_{eqParallel} = \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)^{-1}$$
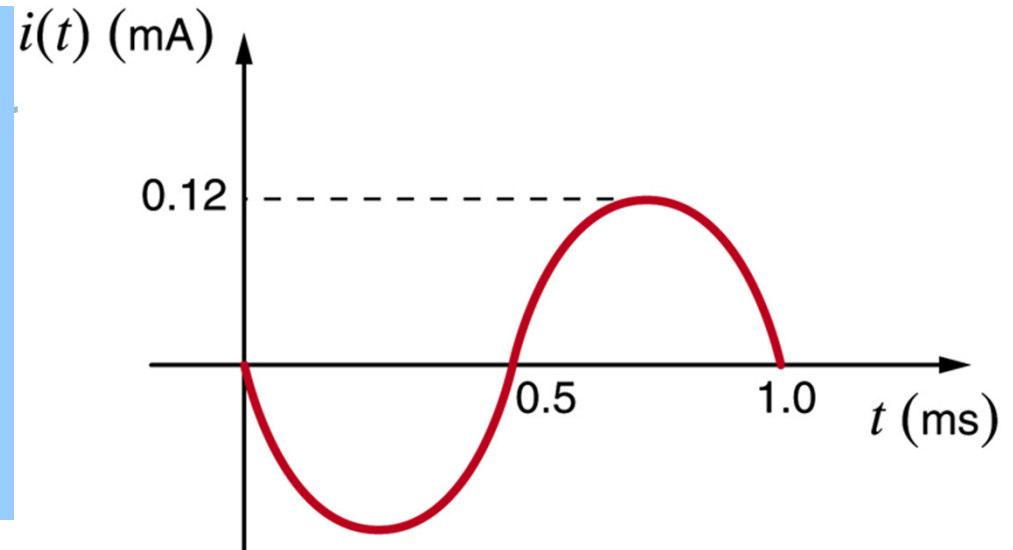
## Clicker

The current through a 1 mH inductor is shown to the right. At which of the following times does the inductor absorb power?



- A.**  $t = 0.1$  ms      **D.**  $t = 0.75$  ms  
**B.**  $t = 0.25$  ms    **E.**  $t = 0.9$  ms  
**C.**  $t = 0.5$  ms