

#1 <10 Marks> ELEC 4602, Test 2, 2016

Given a 50 KVA, 2400 – 240 volt single-phase transformer.

The 240 volt winding is short-circuited and 48 volts is applied to the 2400 volt winding.

Current and power input are measured at the 2400 volt winding. Results as follows:

Voltage = 48 volts

Current = 20.8 amps

Power = 620 watts,


The nameplate indicates that the no-load loss is 186 watts.

Determine the voltage regulation and efficiency of the transformer when supplying rated load, 50 KVA at 240 volts and 0.80 lagging power factor.

$$R_{eH} = \frac{P_u}{I_u^2} = \frac{620}{20.8^2} = \underline{\underline{1.43 \Omega}} \quad (1)$$

$$Z_{eH} = \frac{V_{sc}}{I_u} = \frac{48}{20.8} = 2.30 \Omega$$
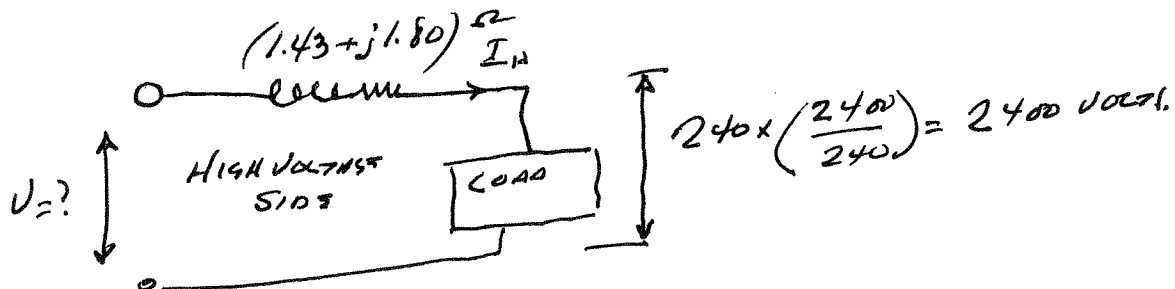
$$\therefore X_{eH} = \sqrt{Z_{eH}^2 - R_{eH}^2} = \sqrt{2.30^2 - 1.43^2} = \underline{\underline{1.80 \Omega}} \quad (2)$$



$$I_H = \frac{50}{2.4} \angle -\cos^{-1} 0.8 = 20.8 \angle -36.87^\circ \text{ AMPS.} \quad (2)$$

NOTE THIS IS ALSO THE TEST AMPS.

$$\therefore V = 2400 \angle 0 + (20.8 \angle -36.87) / (1.43 + j 1.80)$$

$$\therefore V = 2446.4 \angle 2 \quad (2)$$

$$\therefore \% \text{ VOLTAGE REGULATION} = \frac{2446.4 - 2400}{2400} \times 100 = \underline{\underline{1.9\%}} \quad (1)$$

$$\text{Power out} : 50,000 \times 0.8 = 40,000 \text{ WATTS}$$


$$\begin{aligned} \text{COPPER LOSS} &= 620 \text{ WATTS (W/1757)} \\ &(\text{OR } 20.8^2 \times 1.43 = 619 \text{ WATTS}) \quad (1) \end{aligned}$$

$$\text{CORE LOSS} = 186 \text{ WATTS}$$

$$\therefore P_{IN} = 40,000 + 620 + 186 = 40,806 \text{ WATTS}$$

$$\therefore \%, \text{ EFFICIENCY} = \frac{40,000}{40,806} \times 100 = \underline{\underline{98\%}} \quad (1)$$

#2 <9 Marks>

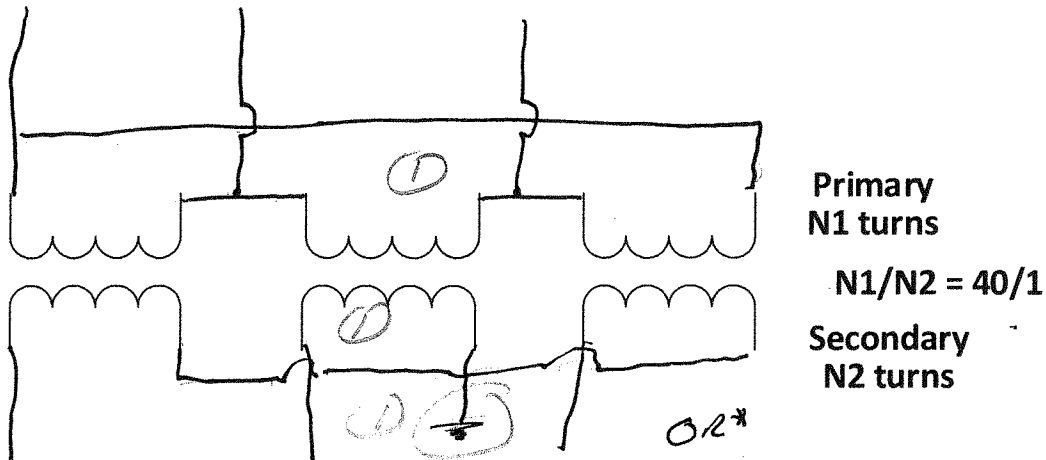


The above transformer bank supplies a balanced three-phase load of 500 kW at 600 volts, line-to-line and 0.90 lagging power factor.

a) Connect the above transformers delta on the primary side and grounded wye on the secondary side. Calculate the magnitude of:

- | | |
|---------------------------------------|-------------|
| b) Secondary line current, | 534.6 AMPS |
| c) Secondary phase current, | 534.6 AMPS |
| d) Secondary line-to-neutral voltage, | 346.4 VOLTS |
| e) Primary voltage, line-to-line, | 13.856 KV |
| f) Primary phase current, | 13.365 AMPS |
| g) Primary line current. | 23.15 AMPS. |

1 MARK EACH.

OR*

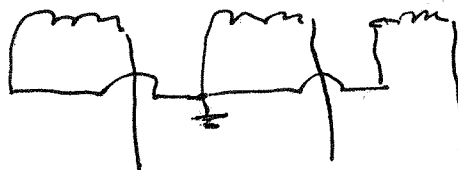

$$(b) P = \sqrt{3} V_{LL} I_L \cos \theta \Rightarrow I_L = \frac{P}{\sqrt{3} V_{LL} \cos \theta} = \frac{5000}{\sqrt{3} \times 0.6 \times 0.9} = \underline{534.6}$$

$$(c) \text{ WYE CONNECTION: } I_L = I_P = \underline{534.6 \text{ AMPS}}$$

$$(d) V_{LN} = \frac{V_{LL}}{\sqrt{3}} = \frac{600}{\sqrt{3}} = \underline{346.4 \text{ VOLTS}}$$


$$(e) \text{ Primary Voltage L-L: } \frac{600}{\sqrt{3}} \times 40 = \underline{13.856 \text{ KV}}$$

$$(f) \text{ Primary Phase current } \frac{534.6}{40} = \underline{13.365 \text{ AMPS}}$$

$$(g) \text{ Primary Line current } 13.365 \times \sqrt{3} = \underline{23.15 \text{ AMPS}}$$

$$\text{CHECK } P = \sqrt{3} \times 13.856 \times 23.15 \times 0.9 = \underline{5000 \text{ KW}}$$

#3 <11 Marks>

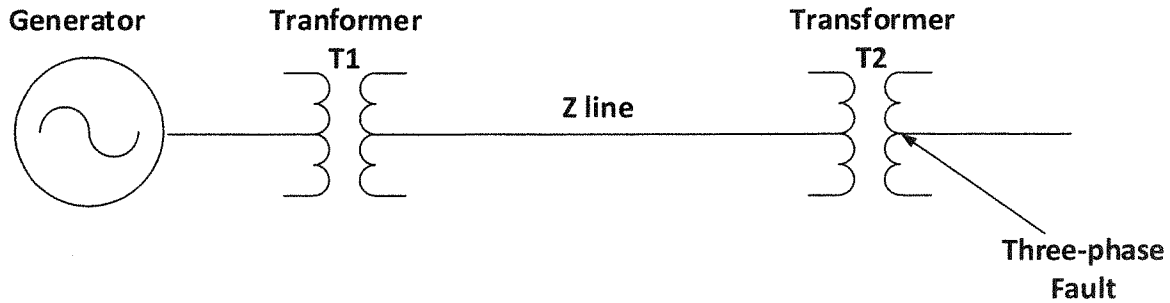

Following are the nameplate data for the three-phase system shown above.

GENERATOR: 50 MVA, 13.8 kV, %IX = 15%
TRANSFORMER T1: 25 MVA, 13.2 – 161 kV, %IX = 10%
Z line: (10 + j10) ohms
TRANSFORMER T2: 15 MVA, 13.8 – 161 kV, %IX = 10%

- Using the per unit method of calculation with basis 100,000 KVA and 13.8 kV, the generator rated voltage, calculate the symmetrical short circuit current and the short circuit KVA for a three-phase fault on the low voltage terminals of transformer T2.
- Calculate the asymmetrical short circuit current.

$$(a) \quad Z_{pu, NEW} = Z_{pu, OLD} \left(\frac{KV_{BASE, OLD}}{KV_{BASE, NEW}} \right)^2 \times \left(\frac{KVA_{BASE, OLD}}{KVA_{BASE, NEW}} \right)$$

GENERATOR:

$$Z_{pu} = 0.15 \left(\frac{13.8}{13.8} \right)^2 \times \left(\frac{100,000}{50,000} \right) = j0.30 \text{ pu} \quad (1)$$

TRANSFORMER T1:

$$Z_{pu} = 0.10 \left(\frac{13.2}{13.8} \right)^2 \left(\frac{100,000}{25,000} \right) = j0.366 \text{ pu} \quad (1)$$

$$\text{LINE: } VOLTAGE \text{ BASE} = \frac{161}{13.2} \times 13.8 = 168.3 \text{ kV.}$$

$$Z_{BASE \text{ LINE}} = \frac{(KV_{BASE})^2 \times 1000}{KVA_{BASE}} = \frac{168.3^2 \times 1000}{100,000} = 283.2 \Omega \quad (1)$$

$$\therefore Z_{pu, LINE} = \frac{10 + j10}{283.2} = (0.035 + j0.035) \text{ pu} \quad (1)$$

TRANSFORMER T2: ($V_{BASE} = 168.3 \text{ kV}$)

$$Z_{pu} = 0.10 \left(\frac{161}{168.3} \right)^2 \times \left(\frac{100,000}{15,000} \right) = j \underline{0.61} \text{ pu} \quad (1)$$

TOTAL PER UNIT IMPEDANCE TO POINT OF FAULT

GENERATOR: $0 + j0.30$

T1 $0 + j0.366$

LINE $0.035 + j0.035$

T2 $0 + j0.61$

$$\text{TOTAL} = 0.035 + j1.311 \Rightarrow \underline{1.311} \text{ pu} \quad (1)$$

$$V_{BUS} \text{ OF FAULT: } \frac{13.8}{101} \times 168.3 = \underline{14.426 \text{ kV}} \quad (1)$$

$$\underline{I_{BASE} \text{ OF FAULT}} = \frac{KVA_{BASE}}{\sqrt{3} KVA_{MISC}} = \frac{100,000}{\sqrt{3} \times 14.426} = \underline{4002 \text{ AMPS}} \quad (1)$$

$$\therefore I_{SC} = \frac{I_{BASE}}{Z_{pu}} = \frac{4002}{1.311} = \underline{3053 \text{ AMPS}} \quad (1)$$

$$\text{SHORT CIRCUIT IWA} = \frac{KVA_{BASE}}{Z_{pu}} = \frac{100,000}{1.311} = \underline{76,278 \text{ IWA}} \quad (1)$$

$$(b) \quad \frac{X}{R} = \frac{1.311}{0.035} = 37.5 \therefore \frac{I'}{I} \approx 1.72$$

$$\downarrow I_{SC, Asym} = 3053 \times 1.72 = \underline{5,251 \text{ AMPS}} \quad (1)$$