

Université d'Ottawa
Faculté de génie
SIGE



uOttawa
L'Université canadienne
Canada's university

University of Ottawa
Faculty of Engineering
EECS

ITI 1100-B

Digital Systems I

Mid-Term Examination

First Name: Ali
Last Name : Karime
Student #: Sample Solution
Signature: _____

Professor: Ali Karime

Exam Duration: 90 minutes

Instructions

- Closed book examination. The maximum score is 100 points.
- Use the provided space to answer the questions. If more space is required, use the back of the page.
- Show all the steps to obtain marks.
- Calculators are **NOT allowed**.
- It is strongly recommended that you write down your solutions step by step. This is the only way it is possible for you to earn full marks.
- Cheating will be penalized in accordance with University of Ottawa regulations.

Question 1	(35)	
Question 2	(10)	
Question 3	(55)	
Total	/100	

(b) Perform the following binary arithmetic operations using **1's complement**.

(i) $C = A - B$ [7.5 points]

(ii) $D = A + B$ [7.5 points]

i) $1's \{ B \} = 1's \{ 010000.10 \} = 101111.01$

$A - B = A + 1's \{ B \}$

$$\begin{array}{r} 001100.01 \\ + 101111.01 \\ \hline \end{array}$$

$$\begin{array}{r} 111011.10 \\ \hline \end{array}$$

Sign 1's complement magnitude form

So the answer in magnitude is -00100.01

ii)
$$\begin{array}{r} 001100.01 \\ + 010000.10 \\ \hline 011100.11 \end{array}$$

(b) Convert the binary number $(10\ 0110.11)_2$ to hexadecimal. [5]

$$\left(\underbrace{0010}_{(2)} \ \underbrace{0110}_{(6)} \ . \ \underbrace{1100}_{(C)} \right)_{16}$$

$$\Rightarrow (100110.11) = (26.C)_{16}$$

Question 2 (10 points)


Consider the following truth table A, B and C are input variables and F is the output function

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$F = 1$
 $F = 0$
 $F = C$
 $F = C'$

4 points for properly determining the value of F at each pair of combinations

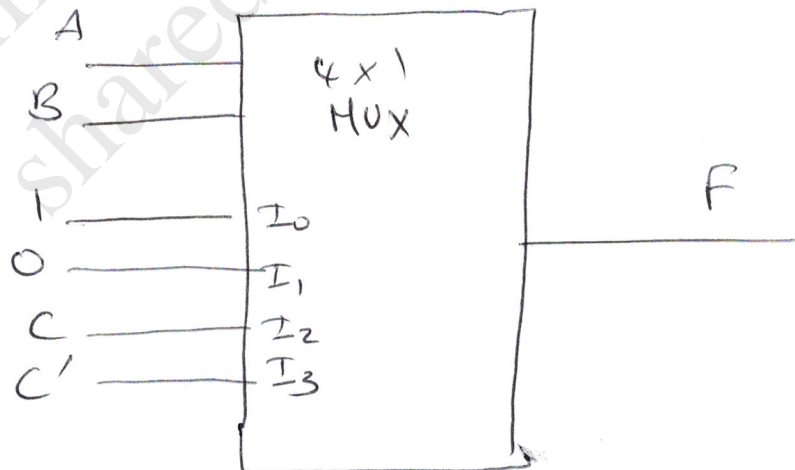a) Implement the function F using a 4-to-1 multiplexer.



6 points for properly drawing the circuit.

Question 3: (55 points)

Given the logic function $F(A,B,C,D) = \Sigma m(1, 3, 5, 12)$ together with the *don't care* conditions $d(A,B,C,D) = \Sigma d(2, 7, 8, 11, 14, 15)$,

- (a) Write the truth table of the logic function. Use the Karnaugh-map method to find the simplest sum-of-products expression of function F . [20 points]

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	X
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	X
1	0	0	0	X
1	0	0	1	0
1	0	1	0	0
1	0	1	1	X
1	1	0	0	1
1	1	0	1	0
1	1	1	0	X
1	1	1	1	X

10 points

AB \ CD	CD			
	00	01	11	10
00	0	1	1	X
01	0	1	X	0
11	1	0	X	X
10	X	0	X	0


the simplified f is not unique


- (1) $F = A'D + Ac'D'$
- or
- (2) $F = A'D + ABD'$

10 pts

Student may give any of the 2 answers.

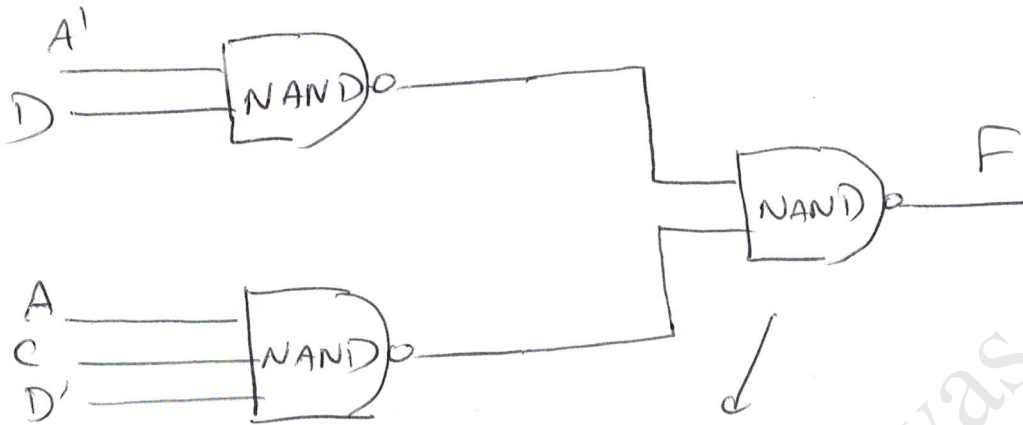- (b) Implement the minimized function with NAND gates only. Note: You can use NAND gates with any number of inputs you may need. Assume, as well, that the input variables are available in both true and complemented form. [10 points]



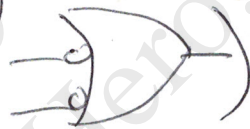(student may use the following symbol here )

10 pts

- (c) Express the same logic function in a product of sums form (give the non-simplified form of the function). [5 points]

Looking in the truth table for the maxterms, we find

$$F = (A + B + C + D)(A + B' + C + D)(A + B' + C' + D)(A' + B + C + D')$$

$$(A' + B + C' + D)(A' + B' + C + D')$$

5 pts

(d) Simplify your function in product of sums. [10 points]

We simplify by grouping 0's first and then finding F'
 (N.B: simplification is not unique)

$$F' = A'D' + AD + AC$$

or $F' = A'D' + AD + AB'$ or $F' = A'D' + AD + CD'$

if $F = A'D' + AD + AC$ is chosen, then

$$F = F'' = (A + D)(A' + D')(A' + C')$$

10pts

(e) Implement your function F employing a 4-to-16 active low decoder (see the following block diagram) and AND gate (with required number of inputs) only. [10 points]

$$F = \Pi(0, 4, 6, 9, 10, 13)$$

10pts

