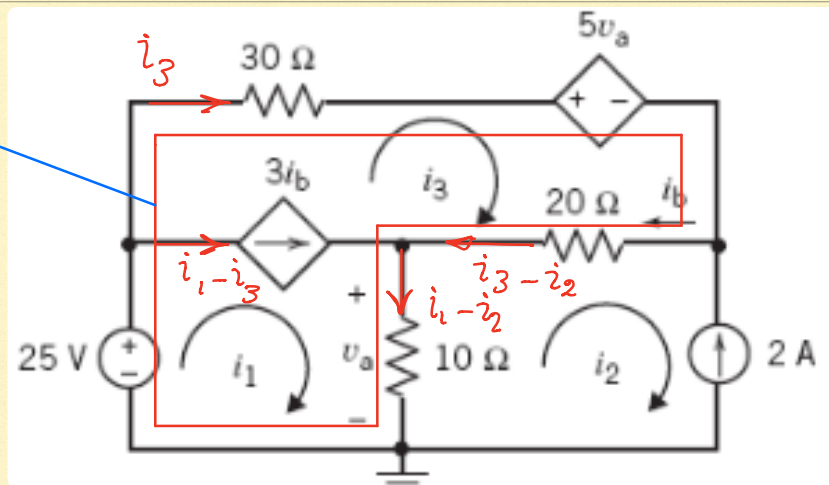


# Solution of assignment by Emad Gad

Supermesh



$$i_2 = -2 \text{ A}$$

— (1)

$$v_a = 10 \times (i_1 - i_2) = 10 i_1 + 20$$

$$i_b = i_3 - i_2 = i_3 + 2$$

KVL of Supermesh:

$$-25 + 30 \times i_3 + 5 \times (10 i_1 + 20) + 20 \times (i_3 - i_2) + 10 \times (i_1 - i_2) = 0$$

— (2)

From the supermesh

$$i_1 - i_3 = 3 i_b$$

$$i_1 - i_3 = 3(i_3 + 2)$$

$$i_1 = 4 i_3 + 6$$


— (3)

Substituting from (3) and (1) into (2) gives  $i_3$

$$i_3 = -1.7069$$

and from (3) we get  $i_1$

$$i_1 = -0.8276$$

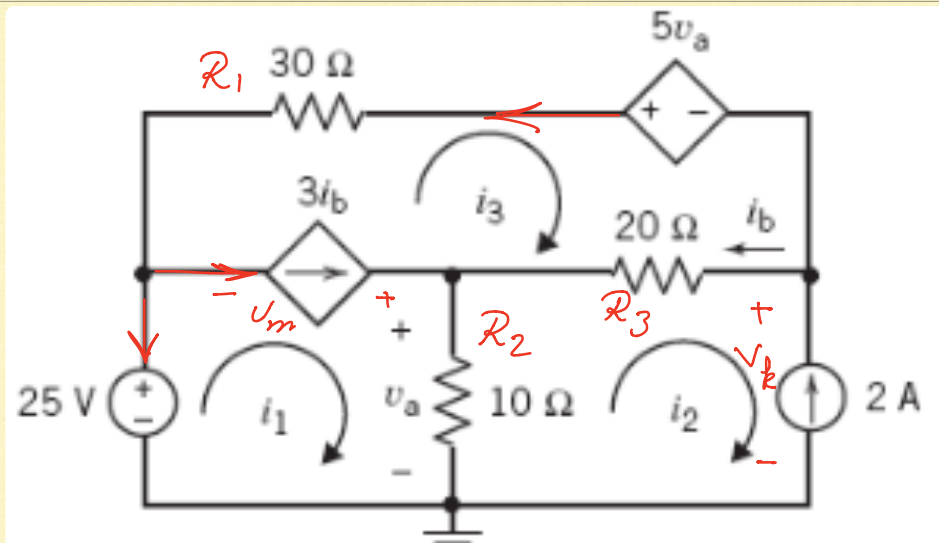

To compute the voltage across the 2A independent source,  $v_k$ , we apply KVL @ mesh (2)

$$-10 \times (i_1 - i_2) - 20 \times (i_3 - i_2) + v_k = 0$$

$$v_k = 10(i_1 - i_2) + 20(i_3 - i_2)$$


$$= 17.58 \text{ V}$$

To compute the voltage across the dependent current source,  $v_m$ , we apply KVL @ mesh (1)

$$-25 - v_m + v_a = 0$$

$$v_m = -25 + v_a = -13.27$$

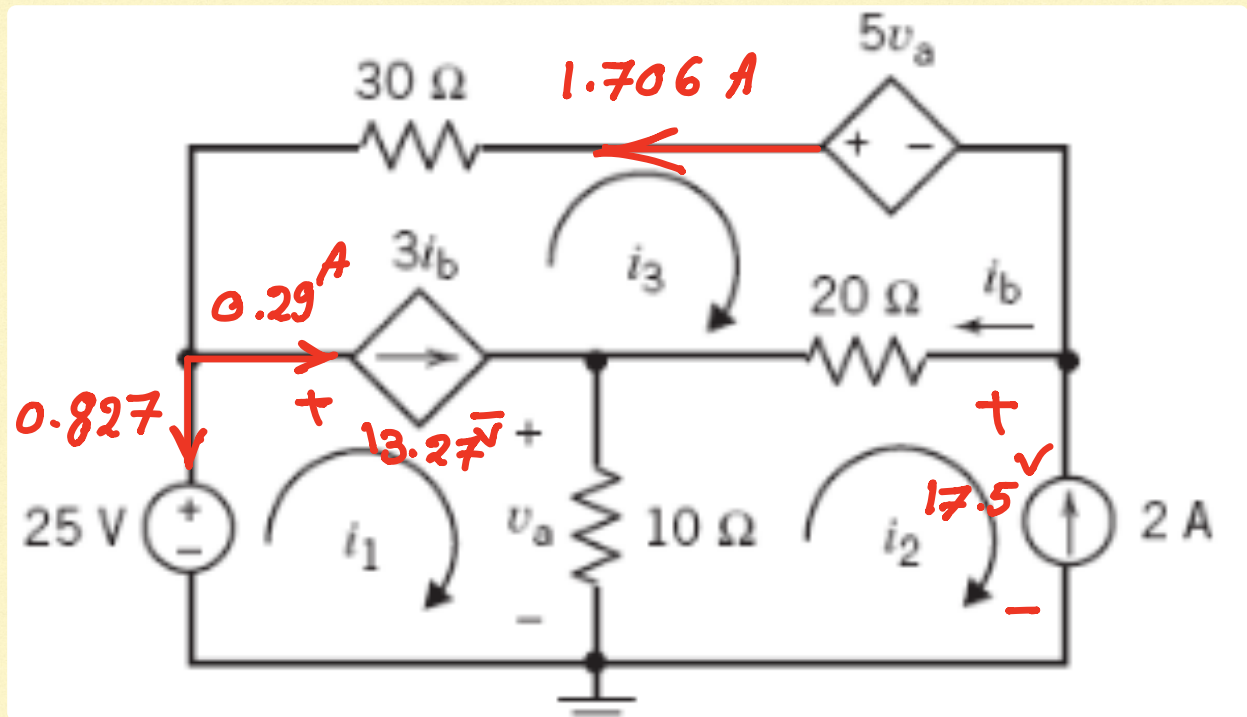We can now place all the values of the voltage and currents in the circuit after adjusting for the signs.



Now we can see that

25 V absorbs power  $\rightarrow 20.68$  W

5 $v_a$  dependent source delivers power  
 $\rightarrow -100$  W

3 $i_b$  dependent source absorbs power  
 $\rightarrow 11.67$  W

2 A source delivers power  $\rightarrow -35.17$  W

$$\begin{aligned} \text{net power} &= \text{net power delivered} - \\ &\quad \text{net power absorbed} \\ &= 102.86 \text{ W} \end{aligned}$$

The power naturally absorbed the resistor must add up to 102.86 W

This is confirmed by the table below.

	A	B	C	D	E
	Element	Current	Voltage	Power (negative for power delivered and positive for power absorbed)	
1					
2	Indendent Voltage Source	0.82758621	25	20.68965517	
3	Indendent Current Source	2	17.5862069	-35.17241379	
4	Dependent Voltage Source	1.70689655	58.6206897	-100.059453	
5	Dependent Current Source	0.87931034	13.2758621	11.67360285	
6	R1	1.70689655		87.40487515	
7	R2	1.17241379		13.74554102	
8	R3	0.29310345		1.718192628	
9	Net Power delivered			-102.8686088	
10	Net Power absorbed by resistors			102.8686088	
11					

Correct